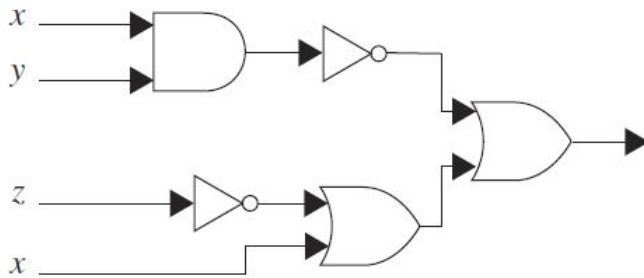


## 12.3 Logic Gates

### 12.3 pg. 827 # 3

Find the output of the given circuit.



### 12.3 pg. 827 # 5

Find the output of the given circuit.

